



LINEAR IC APPLICATIONS LAB


M. Vanitha

Assistant Professor


Department of ECE

Jyothishmathi Institute of Technology & Science

Contents

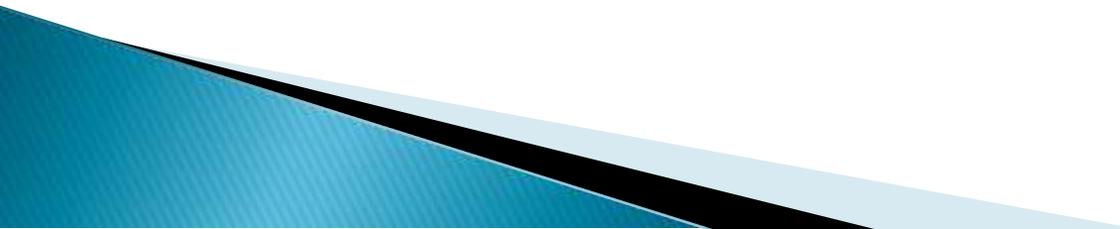- ▶ 1. Block diagram of op amp
 - ▶ 2. Circuit diagram
 - ▶ 3. Input/output waveforms
 - ▶ 4. Advantages and Disadvantages
 - ▶ 5. Features
 - ▶ 6. Applications
- 

Block Diagram of Op-Amp

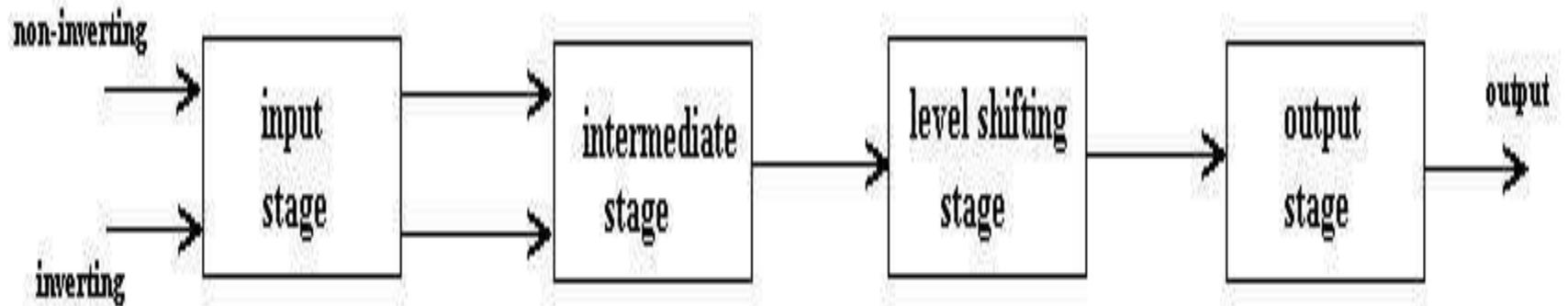

Inverting and Non-inverting Amplifiers using Op Amps


Aim

To design and setup an inverting amplifier and a non-inverting amplifier circuit with Op Amp 741, plot the waveforms, observe the phase reversal, measure the gain.


Apparatus

- ▶ IC 741
- ▶ Resistors (1K Ω ,10K Ω)
- ▶ Function generator
- ▶ Regulated power supply
- ▶ IC bread board trainer
- ▶ CRO
- ▶ Patch cards and CRO probes

Circuit Diagram

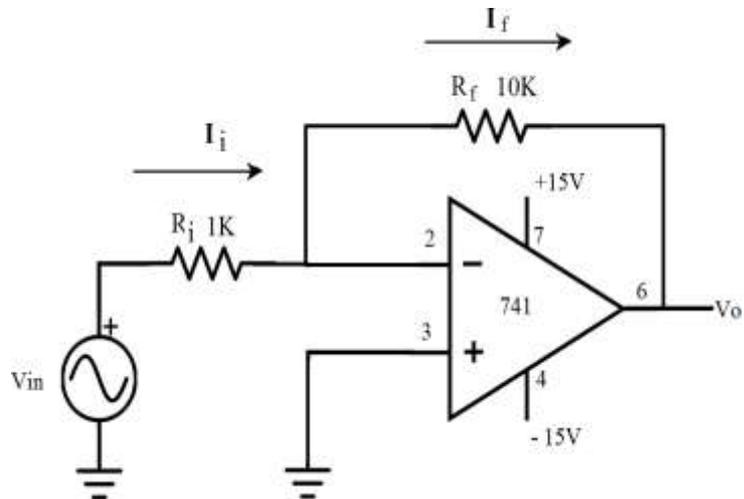





Inverting
Amplifier

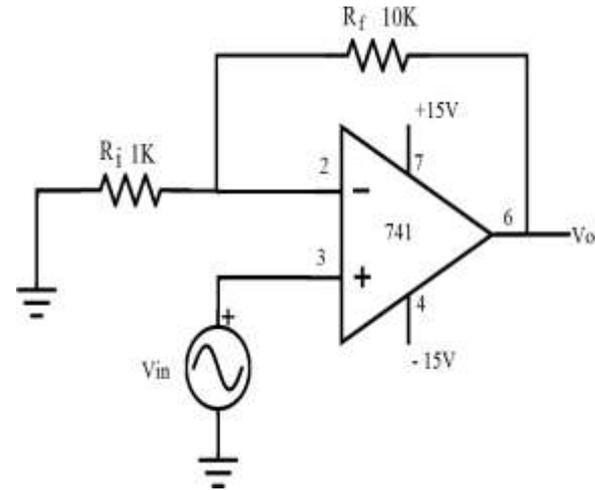

Non Inverting
Amplifier


Input & Output Waveforms

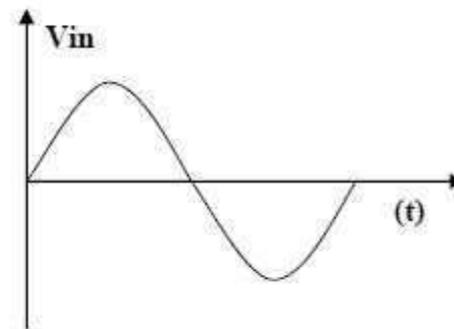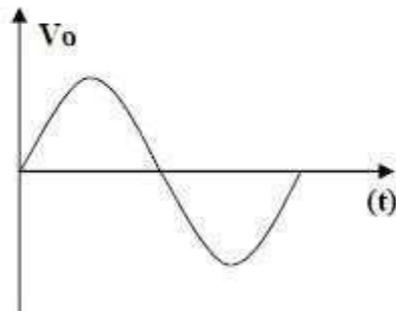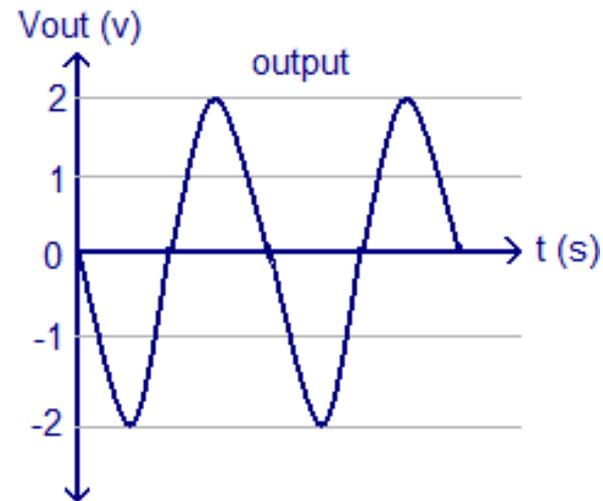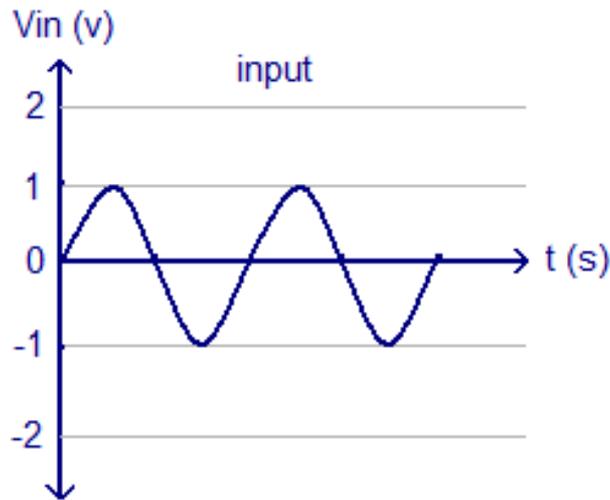Input and output waveforms of an opamp inverting amplifier (gain assumed to be 2)




Output: Non- Inverting Amplifier


Advantages of op Amp

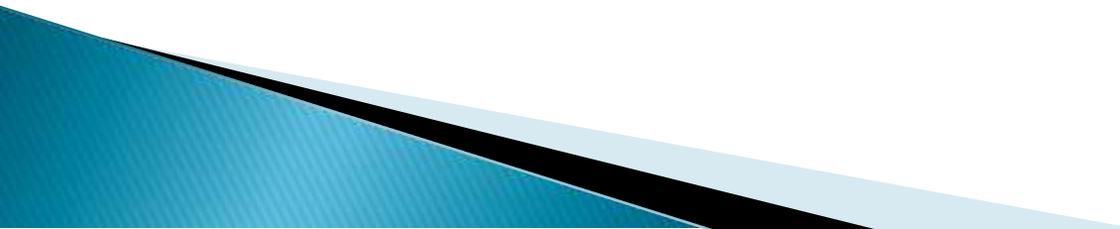- ▶ Op amp is an universal amplifier
 - Analog to digital converter
 - ▶ Low value feedback Resistors to reduce noise
 - ▶ High input impedance
- 


Disadvantages of Op Amp

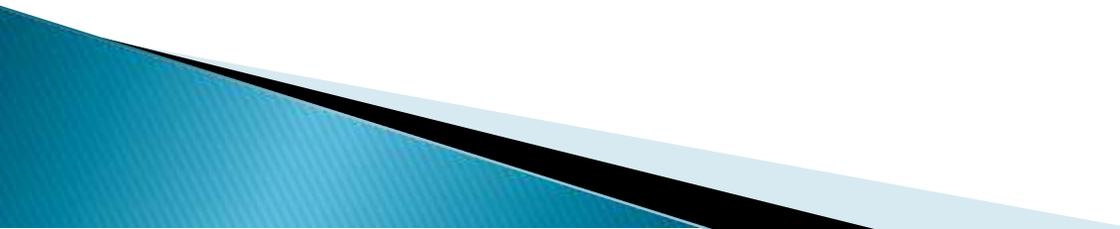- ▶ Most Op Amp are designed to for lower power operation
 - ▶ For high output is desired then the Op Amp specifically designed for that purpose must be seen
 - ▶ Most commercial Op Amp shuts off when the load resistances is below a specific level
- 

Features of IC 741

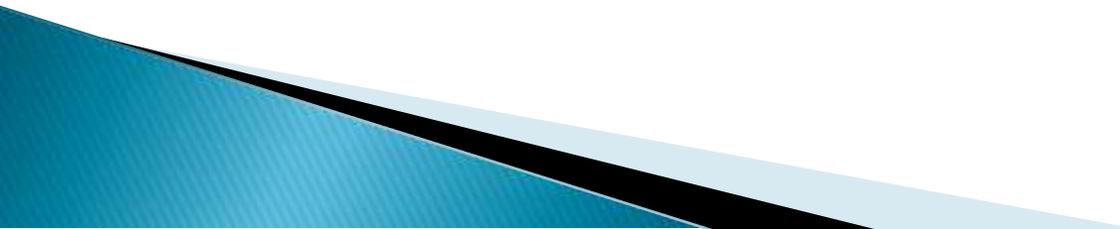- ▶ No frequency compensation required.
 - ▶ Short circuit protection.
 - ▶ Offset voltage null capability.
 - ▶ Large common mode and differential voltage ranges.
 - ▶ Monostable and Bistable operation.
- 

Applications of IC 741

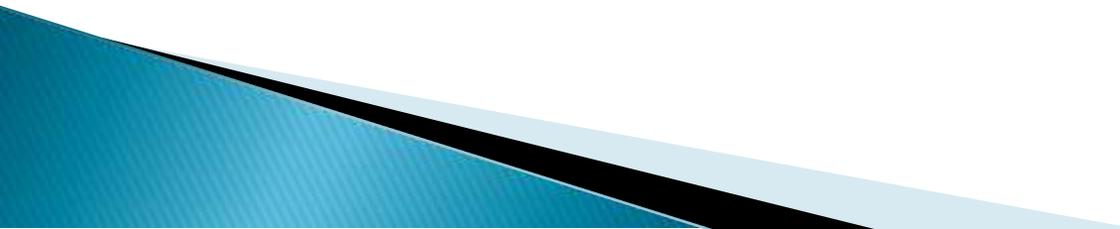- ▶ AC and DC amplifiers
 - ▶ Active filters
 - ▶ Oscillators
 - ▶ Rectifiers
 - ▶ comparators
- 

THANK YOU

