



**JYOTHISHMATHI INSTITUTE OF TECHNOLOGY AND SCIENCE**

# **TOPIC: Combinational Circuits**

## **Sub: Switching Theory and Logic Design**

By

Nuthi.Raju

Asst.Prof

Dept. Of ECE.

# Combinational Circuits




A combinational  
<sup>n</sup> circuits

of input values

- 2 possible combinations

n input  
variables

 

m output  
variables

- Specific functions

- ◆ Adders, subtractors, comparators, decoders, encoders, and multiplexers


- ◆ MSI circuits or standard cells

# Analysis Procedure

- ◆ Step 1: Label all gate outputs that are a function of input variables with arbitrary symbols – but with meaningful names. Determine the Boolean functions for each gate output.
- ◆ Step 2: Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Find the Boolean functions for these gates.
- ◆ Step 3: Repeat the process outlined in step 2 until the outputs of the circuit are obtained.
- ◆ Step 4: By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables.

# Analysis Procedure Example

- ◆ A straight-forward procedure

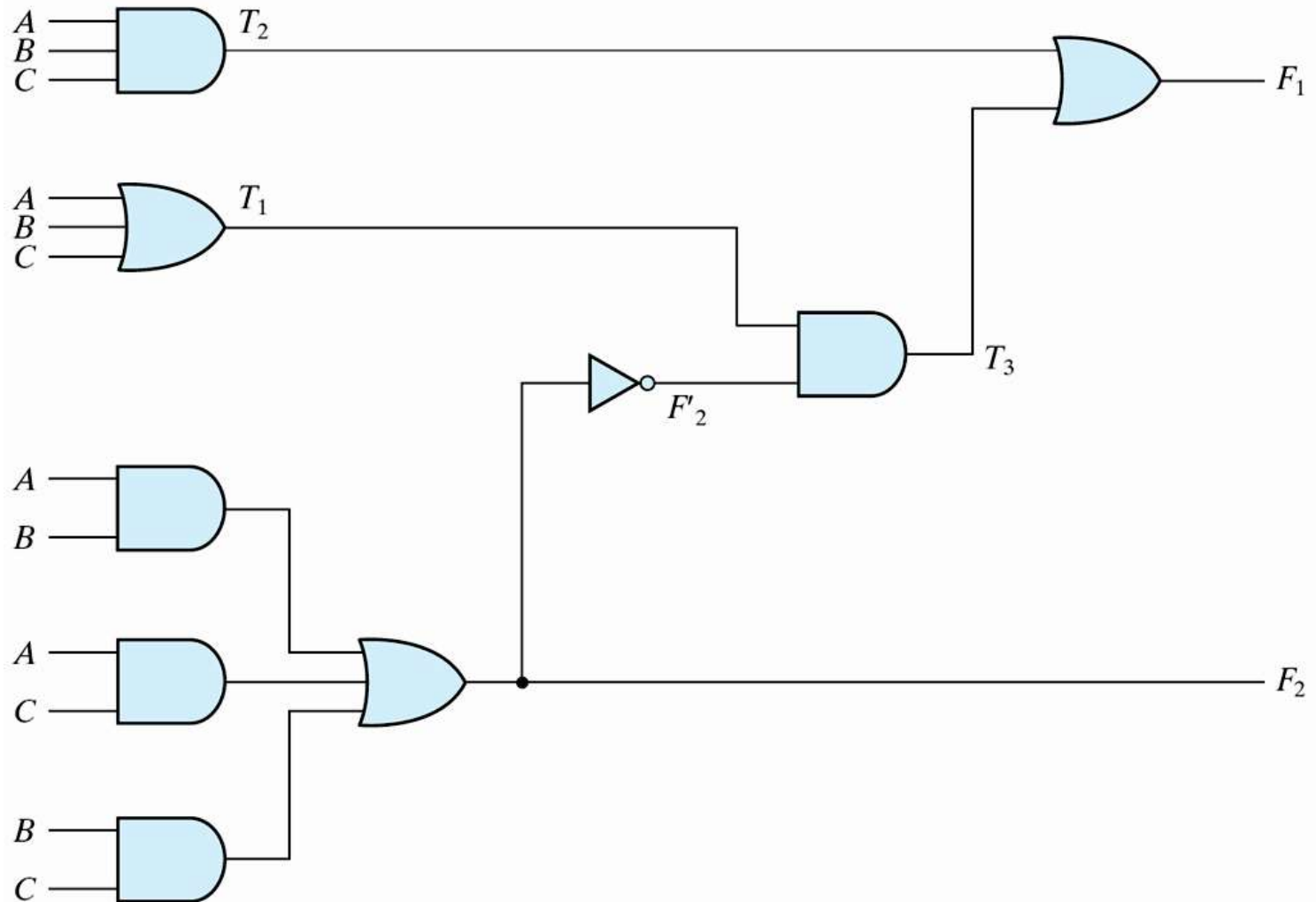

# Analysis Procedure Example

## ◆ Step 1:

- $F_2 = AB+AC+BC$
- $T_1 = A+B+C$
- $T_2 = ABC$

## ◆ Ste 2:

- p
- $T_3 = F_2'T_1$

## ◆ Step 3:

- $F_1 = T_3+T_2$

## ◆ Step 4:

- $$\begin{aligned} F_1 &= T_3+T_2 = F_2'T_1+ABC \\ &= (AB+AC+BC)'(A+B+C)+ABC \\ &= (A'+B')(A'+C')(B'+C')(A+B+C)+ABC \\ &= (A'+B'C')(AB'+AC'+BC'+B'C)+ABC \\ &= A'BC'+A'B'C+AB'C'+ABC \end{aligned}$$

# Truth Table

**Table 4.1**

*Truth Table for the Logic Diagram of Fig. 4.2*

<b>A</b>	<b>B</b>	<b>C</b>	<b>F<sub>2</sub></b>	<b>F'<sub>2</sub></b>	<b>T<sub>1</sub></b>	<b>T<sub>2</sub></b>	<b>T<sub>3</sub></b>	<b>F<sub>1</sub></b>
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

# Decoder

## ◆ An $n$ -to- $m$ decoder

- a binary code of  $n$  bits =  $2^n$  distinct information
- $n$  input variables; up to  $2^n$  output lines
- only one output can be active (high) at any time

**Table 4.6**


*Truth Table of a Three-to-Eight-Line Decoder*

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# 4x16 Decoder

## ◆ Expansion


- two 3-to-8 decoder: a 4-to-16 decoder

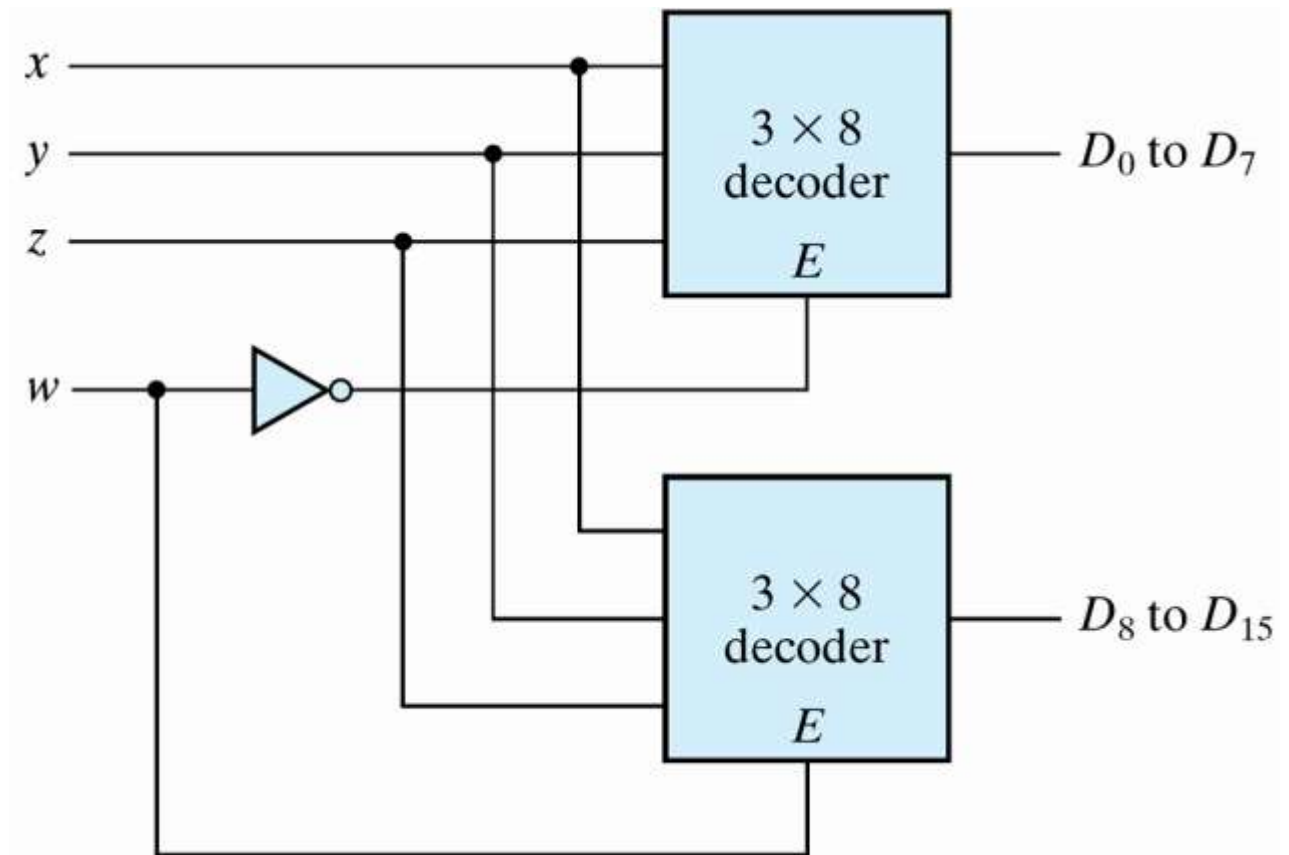

4 × 16 decoder  
constructed with two  
3 × 8 decoders



# 4-to-1-Line Multiplexer

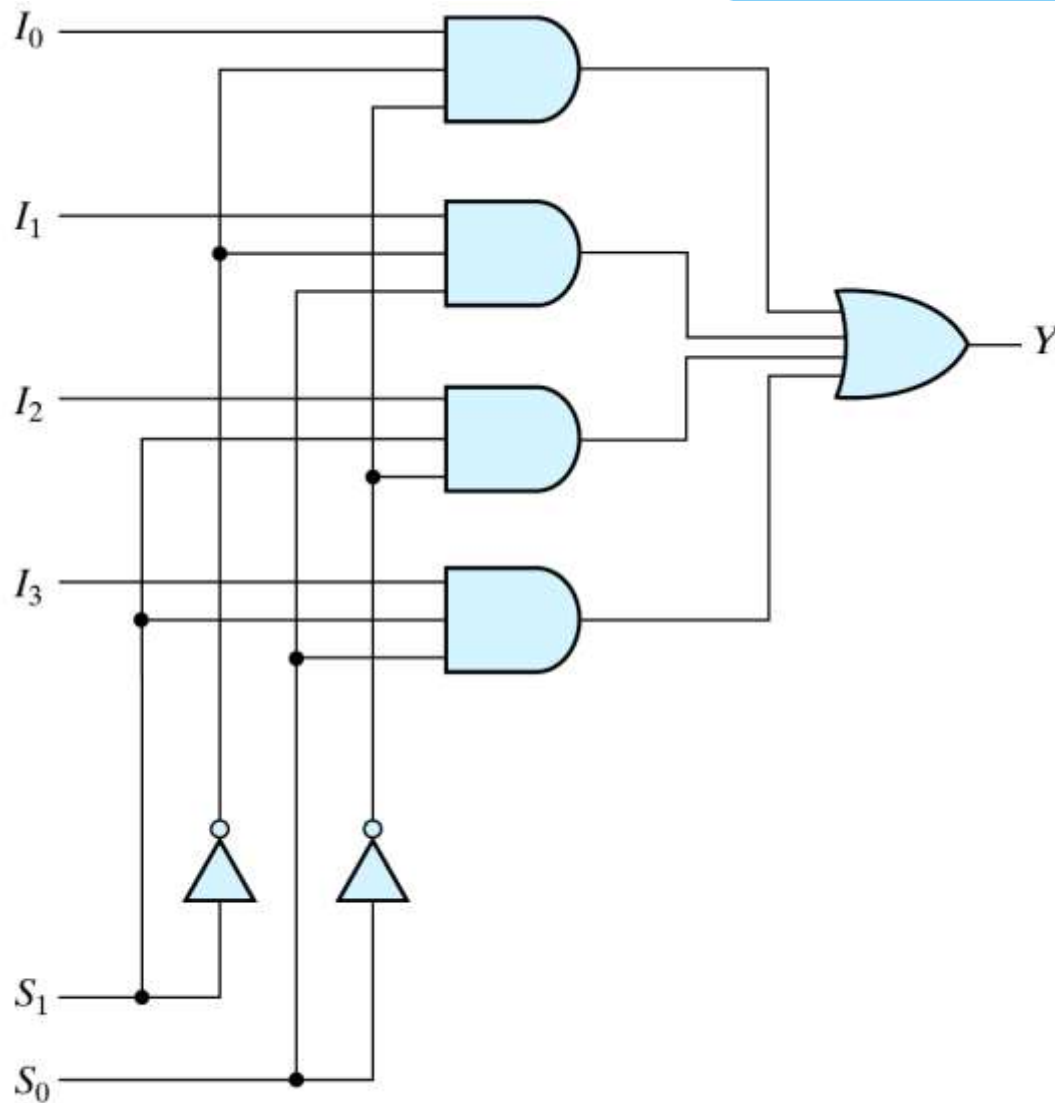

(a) Logic diagram

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table