

# Full Wave Rectifier with & without filters

CH.LAVANYA

Assistant professor

Department of BCE

Jyothishmathi Institute of Technology & Science

#### **ELECTRONIC COMPONENTS**

- ACTIVE COMPONENTS
- PASSIVE COMPONENTS

## ACTIVE COMPONENTS

- THE ELECTRONIC COMPONENTS WHICH ARE CAPABLE OF AMPLIFYING AND PROCESSING ON ELECTRICAL SIGNAL ARE CALLED ACTIVE COMPONENTS
- EXAMPLES
- TRANSISTORS
- LOGIC GATES

## PASSIVE COMPONENT

- THE ELECTRONIC COMPONENTS WHICH ARE NOT CAPABLE OF AMPLIFYING OR PROCESSINFG AN ELECTRICAL SIGNAL ARE CALLED PASSIVE COMPONENTS.
- EXAMPLES
- RESISTOR
- CAPACITOR
- INDUCTOR


### Full Wave Rectifier with & without filters

• **AIM:**-To find the Ripple factor and regulation of a Full-wave Rectifier with and without filter.

#### • <u>APPARATUS</u>:-

- Experimental Board
- Transformer (6-0-6v).
- P-n Diodes, (IN4007) ---2 No's
- Multimeters –2No's
- Filter Capacitor (100µF/25v) -
- Connecting Wires
- Load resistor, 1KΩ
- •

## **CIRCUIT DIAGRAM**

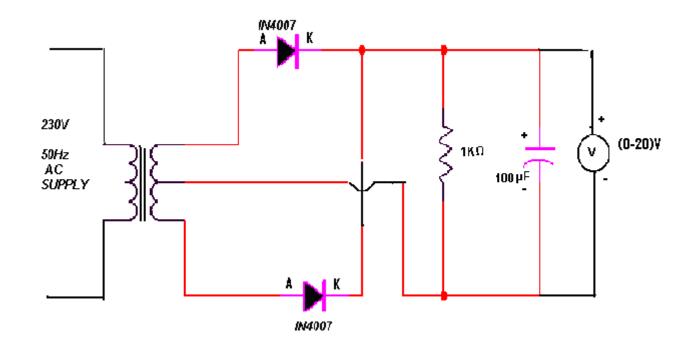

#### • **PROCEDURE**:

- Connections are made as per the circuit diagram.
- Connect the ac mains to the primary side of the transformer and the secondary side to the rectifier.
- Measure the ac voltage at the input side of the rectifier.
- Measure both ac and dc voltages at the output side the rectifier.
- Find the theoretical value of the dc voltage by using the formula  $Vdc=2Vm/\Pi$
- Connect the filter capacitor across the load resistor and measure the values of Vac and Vdc at the output.
- The theoretical values of Ripple factors with and without capacitor are calculated.
- From the values of Vac and Vdc practical values of Ripple factors are calculated. The practical values are compared with theoretical values.

#### • **PRECAUTIONS:**

- The primary and secondary side of the transformer should be carefully identified
- The polarities of all the diodes should be carefully identified.

"Remember to look up at the stars and not down at your feet. Try to make sense of what you see and wonder about what makes the universe exist. Be curious. And however difficult life may seem, there is always something you can do and succeed at. It matters that you don't just give up."

- Prof Stephen Hawking

## Thank you!!